

MORNING

30 DEC 2022
[Total No. of Pages: 02]

[Total No. of Questions: 09]

Uni. Roll No.

Program: B.Tech. (Batch 2018 onward)

Semester: 3

Name of Subject: Electronic Devices

Subject Code: PCEC-101

Paper ID: 16031

Scientific calculator is Allowed.

Detail of allowed codes/charts/tables etc. Not Required.

Time Allowed: 03 Hours

Max. Marks: 60

NOTE:

- 1) Parts A and B are compulsory
- 2) Part-C has Two Questions Q8 and Q9. Both are compulsory, but with internal choice
- 3) Any missing data may be assumed appropriately

Part – A

[Marks: 02 each]

Q1

- (a) Compare intrinsic semiconductors and extrinsic semiconductors.
- (b) Define operating point in transistors.
- (c) Show the ideal V-I characteristics of p-n junction diode with the help of graph.
- (d) Explain various hybrid parameters in h-equivalent circuit of a two-port network.
- (e) A transistor having $\alpha=0.975$ and reverse saturation current $I_{CO}=10\mu A$, is operated in CE configuration. Determine β for this configuration. If the base current is $250\mu A$, evaluate the emitter current.
- (f) At 300K, the intrinsic carrier concentration of Silicon is $1.5 \times 10^{16} m^{-3}$. If the electron and hole mobilities are 0.13 and $0.05 m^2/(V-s)$ respectively, determine the intrinsic resistivity of silicon at 300K.

Part – B

[Marks: 04 each]

- Q2. Distinguish between LEDs and photodiodes.
- Q3. Develop the relation between conductivity and carrier mobility in a semiconductor.
- Q4. Illustrate any one bias stabilization technique in transistors.
- Q5. Examine the operation of UJT with respect to applied external voltage.
- Q6. An n-channel JFET has $I_{DSS}=12mA$ and pinch-off voltage $V_P=-4V$. Evaluate the drain current for $V_{GS}=-2V$. If the transconductance g_{m0} of a JFET with the same I_{DSS} at $V_{GS}=0$ is 4 millimho, Determine the pinch-off voltage.

Q7. A transistor amplifier in CE configuration couples a source of internal resistance $1\text{k}\Omega$ to a load of $20\text{k}\Omega$. Determine the input and output resistances, if $h_{ie} = 1\text{k}\Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{fe} = 150$ and $1/h_{oe} = 40\text{k}\Omega$.

MORNING

Part – C

[Marks: 12 each]

20 DEC 2022

Q8. Compare half wave rectifiers and full wave rectifiers.

OR

Explain the input and output characteristics of n-p-n transistor connected in common base configuration.

Q9. Classify and explain the working and characteristics of MOSFETs.

OR

Analyze Common emitter transistor amplifier using h-parameters in terms of:

- (i) Input impedance,
- (ii) Output impedance,
- (iii) Current Gain,
- (iv) Voltage Gain.
